Thermostat system

Student: Veliciu Vlad

Group: 2031

Coordinator: Şl. dr. ing. Pătărău Toma

Faculty: Electronics, Telecommunications, and Information Technology

Contents


1.	Intr	oduction	3
2.	Bloc	ck Diagram	4
3.	The	temperature sensor	5
3	3.1.	Main types of temperature sensors	5
3	3.2.	Choosing the temperature sensor: Semiconductor based ICs temperature sensor	7
4.	The	humidity sensor	8
4	l.1.	Main types of humidity sensors	8
2	1.2.	Choosing the humidity sensor: Capacitive humidity sensor	10
5.	Con	necting the analog temperature sensor	11
į	5.1.	Types of ADC	11
į	5.2.	Simulating in Proteus	16
6.	Fun	ctioning of the LCD	18
6	5.1.	How does the LCD work?	18
6	5.2.	Commands for the LCD	20
6	5.3.	Implementation in Proteus	21
7.	Cho	osing the microcontroller	23
8.	Imp	lementing the schematic	26
8	3.1.	Complete electrical schematic in Proteus	26
8	3.2.	Code implementation	29
8	3.3.	Simulation	49
9.	Refe	erences	50

1. Introduction

The aim of this project is to simulate a thermostat system based on a microcontroller, having a temperature sensor which has an analog output, a humidity sensor having a digital output, an LCD where the information about the current temperature and the desired temperature is displayed. Also, an analog-to-digital converter is present in order to transform the output voltage from the analog temperature sensor into a digital format that can be used by the microcontroller. The microcontroller will further compare this temperature with the desired one and will choose whether or not to give information to the heating system to turn on.

The simulations are done in Proteus 8.13 and the code for the microcontroller is written in Keil μ Vision5, in assembly as well as in C language.

2. Block Diagram

 

(fig 2.1: block diagram)


The block diagram shows the connections that are made with the microcontroller. As there can be seen, the microcontroller gets information from the temperature sensor, humidity sensor and the keyboard. The temperature sensor informs about the current room temperature and the keyboard represents the user input (e.g., the desired temperature). As outputs of the microcontroller there are the LCD for displaying information about the real and desired temperature, the humidity and the command to the heating system (activated when the real temperature is below the desired one).

3. The temperature sensor

3.1. Main types of temperature sensors

A. Thermocouples


These sensors have a wide temperature range (-180°C - 2320°C) and quick response times. They are made by joining 2 dissimilar conducting metal wires, causing a Seebeck effect (a temperature difference of 2 different type of wires causes a voltage difference that is used to calculate the temperature). A disadvantage is the small output voltage which can cause problems in measuring the temperature. This means that precise amplification is required and that external noise over the wires can affect the result. Moreover, cold junction appears between the thermocouple wires and the wires of the external circuit that causes another Seebeck effect that must be compensated. There are integrated solutions (with precise ADC, low noise, and compensation of the cold junction). [2]

 

(fig 3.1.1: functioning of thermocouple)

 B. Resistance temperature detector

This sensor is based on the fact that the resistance increases as temperature increases and the resistance vs temperature relationship is known for any material. Platinum is the most material used for building such a sensor because this material offers an almost linear response to temperature changes, is stable and accurate and offers a wide range. This sensor is suitable for low ranges (-200°C - 500°C). There are 2,3 or 4 wires configurations available, depending on the accuracy needed. [2]





RTD Resistance versus Temperature

(fig 3.1.2: Resistance vs Temperature characteristic for different materials for RTD)

C. Thermistors

This type of sensor is like the previous type (dependency much stronger, a change in temperature causes change in resistance that is measurable, but most used thermistors are that whose resistances that increase when temperature decays -> negative temperature coefficient thermistor). They are cheaper but less accurate than resistance temperature detectors and have a non-linear resistance vs temperature characteristic. It is commonly used in a voltage divider configuration with an ADC. [2]

 

 

(fig 3.1.3: Resistance vs Temperature characteristic for thermistors)

D. Semiconductor based ICs

This sensor works with dual ICs. They contain 2 similar diodes (or transistors) with temperature-sensitive voltage and current characteristics to measure the temperature changes effectively. They give a linear output, are sensitive, but are less accurate at 1°C-5°C and have slow responsiveness (5s - 60s). Range is between -70°C - 150°C. [2]

3.2. <u>Choosing the temperature sensor: Semiconductor based ICs temperature</u> sensor

The chosen type of temperature sensor is semiconductor-based IC temperature sensor because of its advantageous size (regular very small size), enough range of temperature for this application (0°C-50°C) and generally gives a digital output.

Types of semiconductor-based I	Cs sensors with	analog output: [1]
--------------------------------	-----------------	--------------------

No.	Name	Temp	Gain	Supply	Supply current	Accuracy	Price
		range (°C)	(mV/°C)	voltage	when measuring	(°C)	(RON)
				(V)	(μΑ)		
1.	TMP236AQDBZRQ1	-10 +125	19.5	3.15.5	14.5	+/-2.5	6.53
2.	MAX6611AUT+T	-40 +125	16	4.55.5	150	+/-1	23.51
3.	MAX6605MXK+T	-55 +125	11.9	2.75.5		+/-0.75	10.00
4.	TMP235A2DBZR	-40 +150	10	2.35.5	15	+/-0.5	6.93
5.	LMT70YFQT	-55 +150	5.194	2.25.5	12	+/-0.2°C	12.73

Considering these five sensors, there can be made some observations regarding which sensor would fit best for this application. Firstly, the required supply voltage is for all sensors equal or below 5V and also the supply current has acceptable values, which is suitable for this application. There can be observed that the parameter "Temperature resolution" would be suitable for the desired temperature range of 0°C-50°C in the case of all sensors. The accuracy though varies from one sensor to another. Knowing that the application refers to a thermostat that regulates the temperature in a room, there is desired that the variance from the real temperature that is measured by the sensor is as low as possible. Consequently, the last one would be more suitable. Moreover, it has to be taken into consideration the gain, so the variation in voltage that would sense of the temperature has changed or not. The gain should be high, so that a difference in voltage can be corrected interpreted as a difference in temperature. However, if the accuracy and gain are taken as decisional criteria between the sensors, the last sensor would be more suitable, although it has a low gain of only 5mV/°C, but its accuracy is high. If the 5mV gain can be successfully measured, this sensor could be used as a temperature sensor in this application, If the accuracy of the measurement of the voltage difference is not so high, the 4th sensor could be used as well.

In conclusion, the sensor used in this application would be **LMT70YFQT**.



(fig 3.2.1: the LM70YFQT sensor)


4. The humidity sensor

4.1. Main types of humidity sensors

A. Capacitive

This sensor measures the relative humidity. It places a thin strip of hygroscopic polymer film between 2 electrodes. The capacity of the metal oxide changes with the atmosphere's relative humidity, this material being hygroscopic. So, the capacitance where this material is used as a dielectric will change because of the dependence of the dielectric to the relative humidity (a function of the ambient temperature and the water vapors pressure). [3]


$$C = \varepsilon * \frac{A}{d}$$
; $\varepsilon = dielectric constant$

 

(fig 4.1.1: structure of a capacitor)

B. Resistive


This type of sensor is made up of materials with relatively low resistivity and the resistivity varies with humidity in an inverse proportional way. The low resistivity material is placed on top of the two electrodes. The contact area between the electrodes and the material has to be increased as much as possible and the resistivity of the material changes when the top layer absorbs water. Commonly used materials are salt, conductive polymers.

 

(fig 4.1.2: structure of a resistive humidity sensor)

C. Thermal conductivity

This type of sensor is used to measure the absolute humidity. It measures the thermal conductivity of dry air and air with water vapors and the difference is referred to as absolute humidity. Two thermistors with negative temperature coefficients are used. One is isolated in a room filled with dry Nitrogen and the other one Is exposed to open air through small venting holes. When powering on the circuit, the resistance of the two are measured and the difference is direct proportional to the absolute humidity. ^[4]

 

(fig 4.1.3: structure of a humidity sensor based on thermal conductivity)

4.2. Choosing the humidity sensor: Capacitive humidity sensor

This type of sensor measures the relative humidity by measuring the changing capacitance.

Types of capacitive humidity sensors with digital output: [1]

No.	Name	Range (% RH)	Supply voltage (V)	Supply current when measuring (µA)	Accuracy (% RH)	Price (RON)
1.	SHT40-AD1B-R3	0 100	1.083.6	320	+/-1.8	12.57
2.	DHT11	20 90	35	500	+/-5	10.85
3.	SHT31-DIS-B2.5kS	0 100	2.45.5	600	+/-2	24.21
4.	HS3004	0 100	3.35.5	7	+/-3.5	12.23
5.	HS3001	0 100	3.35.5	24.4	+/-1.5	32.92

From these sensors, it can be seen that all would provide a good power consumption (V*I) for this application. The range also is wide enough for displaying the humidity in a room (the DHT11 has a slightly narrower range, but acceptable though). The accuracy although is different from one sensor to another and if the price is also taken into account, the conclusion would be that the first sensor is more suitable.

Consequently, the humidity sensor used would be SHT40-AD1B-R3.



(fig 4.2.1: the SHT40-AD1B-R3 sensor)

5. Connecting the analog temperature sensor


For connecting the temperature sensor which has an analog output to the microcontroller, between the sensor and the microcontroller there has to be placed an analog-to-digital converter (ADC) and, if necessary, also an amplifier. The amplification of the amplifier depends on the gain of the sensor (given in mV/°C) and the voltage corresponding to a LSB of the ADC, so that the analog-to-digital converter is able to detect any change noticed by the temperature sensor.

First, the analog-to-digital converter on 8 bits has to be chosen. This means that the converter is able to give at the output 256 (2^8) numbers.

5.1. Types of ADC

A. Flash:

It uses a number of n-1 (n=number of bits) comparators, comparing the input analog voltage to a fraction of Vref. This converter has a high conversion time (depending on the propagation time), but a low resolution that is affected by the non-idealities of the components (e.g. offset of the comparators) ^[5].

 


(fig 5.1.1: structure of flash ADC)

B. ADC implemented with counter:

This type of converter uses a counter that can only count up, together with a DAC and a comparator. The counter practically will count up until the corresponding voltage given by the

DAC reaches the analog input voltage (comparison made with the comparator between the output voltage of the DAC and the Vin) $^{[5]}$. The main drawback is that after every conversion the counter is reset and the duration of the conversions vary, maximum being $2^n * T_{Clk}$, n=number of bits.

 


(fig 5.1.2: structure of ADC w counter)

C. ADC implemented with up/down counter:

It is similar to the previous version, but it is implemented with a counter that can count up and down. This means that the voltage corresponding to every conversion will try to stick to the analog voltage and the time will be the same for all conversions $^{[5]}$, having one at every T_{Clk} . The drawback is that the binary output is never stable, it changes at every clock pulse.

D. ADC with Successive Approximation Registers (SAR)

This converter uses a successive approximation register instead of the counter. The SAR will get the result by dividing in every clock pulse the analog interval in two and setting bit by bit the result. So, at every clock pulse it will know if it has been below or above the analog voltage and will set the bit accordingly $^{[5]}$ (1 if below, 0 if above). It facilitates thus a time that is the same for every conversion, $n * T_{Clk}$, n=number of bits. This represents an advantage because the digital device that will use the result will know the time interval in which a result is ready. It needs though a Sample and Hold circuit so that the analog signal will not vary during the conversion to achieve a reliable result.

 

(fig 5.1.3: structure of ADC w SAR)

Consequently, the type of ADC chosen will be ADC with SAR. The device is **ADC0808**. It has a high impedance chopper stabilized comparator, a 256R voltage divider with analog switch tree and a successive approximation register. The ADC0808 offers high speed, high accuracy, minimal temperature dependence, excellent long-term accuracy, and repeatability, and consumes minimal power. [6] The main characteristics are:

Power: 15 mW (low)

Conversion time: 100 µs


Voltage Supply: 4.5V ... 6V (typical 5V) (VREF + = 5V and VREF - = 0V)

Total error: +/- 0.5 LSB


Input current: 0.5 μA

Output characteristics: the switch in the binary output is made by averaging, not by truncating.


Clock frequency: 640 kHz [6]

 

(fig 5.1.4: transfer characteristics)

 

Timing Diagram

 

(fig 5.1.6: timing for ADC)

From fig 5.1.6 there can be seen that, in order to start the conversion on the START pin, there have to be a pulse of width equal to the period of the clock signal and the signal EOC will signalize the end of conversion only when it gets from LOW level to HIGH level. The OE (Output enable) signal specifies when it is high that the result can be read from the output lines.

Knowing that the voltage corresponding to the least significant bit (input analog voltage that senses a change) is $V_{LSB} = \frac{V_{FS}}{2^N} = \frac{V_{Ref}}{2^8} = 20 mV \ (0.0195V)$ and that the sensor has a gain of approximately 10 mV/°C ^[7] (sensor chosen for simulating in Proteus is **LM45**, as it has characteristics close to the one chosen previously). Also, the voltage corresponding to 0°C is 0V and that corresponding to 50°C gives 0.5V at the output of the sensor ^[7]. Hence in order for the


ADC to give a result that covers the interval of interest for this application, namely 0°C -> 00h and 50°C -> FFh (255), the output voltage from the sensor needs to be amplified before it enters the ADC. The voltage that gives FFh at the output of the ADC is 255*VLSB = 4.99V. This means that the output voltage from the sensor (its maximum value of 0.5V) needs to be amplified 4.99/0.5=9.98 times (approximatively). The next step is to choose an OpAmp that will be put in a non-inverting configuration to achieve this gain.

The most important aspect when choosing an operational amplifier to be used as an amplifier in this configuration is related to the offset voltage and bias currents which can cause an error at the output, especially when there are small voltages such as it is the case in this application. The effect of the biasing currents can be reduced by having equal resistances seen at both inverting and non-inverting input of the OpAmp. Consequently, the offset voltage represents a problem, such that the main criteria when choosing the OpAmp would be that it should have low offset voltage. The response time of the sensor is about 30µs, which is sufficient for the application, as the temperature in a room doesn't vary so fast. This means also that the slew rate of the OpAmp doesn't affect the relation voltage-temperature. Also, the OpAmp should be rail-to-rail (Vout can reach as high as the power supplies) and single-power one.

The chosen OpAmp is **AD8603** ^[1]. It has a very low offset voltage ($50\mu V$), which would give at the output an error of approx. $500\mu V$ (at an amplification of 10). This is far smaller than VLSB, meaning that the correct conversion of the ADC is not affected. Furthermore, it has single-supply operation (1.8V-5V), is a precision amplifier (can amplify small voltages, as it is the case for the voltages at the output of the sensor) and has a high CMRR of 100dB (it can reduce very effectively the noise that can appear between the sensor and the amplifier). Also, it is a rail-to-rail amplifier. ^[8]



(fig 5.1.7: AD8603)

 

(fig 5.1.8: schematic of a non-inverting amplifier)

The configuration from above will be used around the AD8603 amplifier. Knowing that the desired gain is about 9.98 and the formula for the gain for the non-inverting amplifier:

$$A = 1 + \frac{R_2}{R_1} = 9.98 = R_2 = 8.98 * R_1 = take R_1 = 1k\Omega \ and R_2 = 8.98k\Omega$$

5.2. Simulating in Proteus

Connecting the pins of the ADC0808 for simulation in Proteus:

INO...IN7 are the inputs where the analog signal is applied.

ADD A, ADD B, ADD C are the addresses that select the corresponding input (e.g. if A=B=C=LOW, then INO is selected and so on)

ALE is required to load the selected lines into the ADC (put to 0 as only one line is used)


VREF+, VREF- are the supplies (+5V/0V)

Clock: clock signal at a frequency of 640kHz

START and EOC pins are connected together so that continuous conversion is allowed.

OUT1...OUT8 (MSB...LSB) are connected to 2 7-segment display.


OE connected to 5V to ensure that every conversion result is given at the output every time.

 

(fig. 5.2.1: schematic in Proteus)

As there can be seen on the schematic, the value of the resistance R2 is slightly different then the value theoretically computed because of other non-idealities. Also, a resistance R3 has been added (whose value is the value of R1||R2) in order to reduce the effect of the bias currents.


1st case:

 

For 50°C => Vout_sensor=0.5V => Vout_opamp=4.99803V => for ADC:

$$Vout_{opamp} = N * V_{LSB} = N = \frac{Vout_{opamp}}{V_{LSB}} = \frac{4.99803V}{0.01953V} = 255$$

2nd case:

 


For 0°C => Vout_sensor=0V => Vout_opamp=0V => for ADC:

$$Vout_{opamp} = N * V_{LSB} = N = \frac{Vout_{opamp}}{V_{LSB}} = 0$$

6. Functioning of the LCD

6.1. How does the LCD work?

LCDs (Liquid Crystal Displays) work on the principle of blocking light. The molecules inside the crystal tend to untwist when electrical current is applied to the liquid crystal. The angle of the top polarizing filter changes, as well as the angle of the light that passes through the polarizing glass. Because at the back of the LCD there is a mirror (reflector), when there is no current the light can pass through the liquid crystal almost at the same angle and through the reflection of the mirror, there is a bright spot created on the LCD. When there is current through the electrodes, the angle of the light changes in such a way that it doesn't reach the mirror (the horizontal polarizer will block it) and thus a dark spot is created on the LCD. [9]

 

(fig 6.1.1: functioning of the LCD)

For displaying the information to the user, an LCD is needed. Most LCDs have 16x2 or 20x2 displays (16 characters on 2 lines or 20 characters on 2 lines). The standard for communication for the most LCDs is HD44780U which is the controller chip that receives data and sends it to the LCD. It can typically have 4 or 8 lines for data bus and 3 lines for control.

The chosen LCD for this application is one with 16x2 display, **LM016L**, which also has the communication standard HD44780U built in it. The signals (which are transmitted on pins) involved in the writing on the LCD as well as their function are explained next (in the order they appear on the LCD) [10]:

- RS (Register Select): when it is low (0), the data is interpreted as a command or instruction for the LCD (position cursor, clear screen, increment cursor and others) and when it is high (1) the data is interpreted as text which is to be displayed on the LCD. There are two 8-bit registers in the HD44780U: instruction register which is selected when RS=0 (commands) and data register, selected when RS=1 (data to display).
- RW (Read/Write): when it is low (0), the information on the data bus is written to the LCD and when it is high (1), it means that the information from the LCD is read.
- *EN (Enable)*: when sending data to the LCD, this line should be *low (0)*, then the other control lines and the data lines can be set. As the lines have the information on them, EN can be set *high (1)* for a minimum period of time (said by the datasheet, in this case, for writing, 230 ns is the minimum time for the width of the signal in high level and the rise/fall time 20 ns). After that period, EN has to be brought in *low (0)* state again.
- 8 data lines denoted D0...D7 (there can be also used only D0...D3 lines, meaning 4-bit mode)

The *RW* and *RS* signals need to be set accordingly (depending on the application), before the *EN* signal is set. Also, the data hold time refers to the minimum time the data lines should be kept unchanged (with the desired data on them) after the *EN* signal is switched to LOW and the data set-up time represents the minimum time the data lines should be kept unchanged before the *EN* signal switches to LOW.

Beside these lines which are pins on the LCD, there are 3 pins more that are actually the first 3 pins. These pins are explained below (in the order they appear on the LCD):

- Vss represents the ground connection (0V)
- *Vdd* represents the supply connection (typically 5V)
- *Vo (Vee)* represents a pin that controls the contrast of the LCD (usually connected through a potentiometer that can vary the voltage seen by Vo between OV and 5V). This pin is not mandatory to be connected [11].

The next table shows the pin connection and their function in short (from datasheet of LM016L):

INTERNAL PIN CONNECTION

Pin No.	Symbol	Level	Fu	inction			
1	Vss	- 1	0V				
2	VDO	-	+5V	Power supply			
3	V _O	-	-				
4	RS	H/L	L: Instruction code input H: Data input				
5	R/W	H/L	H: Data read (LCD module →MPU L: Data write (LCD module ←MPU				
6	Ε	н, н→∟	Enable signal				
7	D80	H/L					
8	DB1	H/L					
9	DB2	H/L					
10	D83	H/L	Data bus line				
11	D84	H/L	Note (1), (2)				
12	D85	H/L					
13	DB6	H/L					
14	DB7	H/L					

(fig. 6.1.2: pin configuration of LM016L)

6.2. <u>Commands for the LCD</u>


There are many commands that can be given to the LCD, but there are also commands that need to be given before using the LCD (initialization). The table below shows how the signals should be set on the corresponding pins in order to execute a certain command (LCD is used in 8-bit mode, writing on 2 lines):

Instruction	RS	R/W	D7	D6	D5	D4	D3	D2	D1	D0	Hex code
											(D7D0)
16x2 LCD (init)	0	0	0	0	1	1	1	0	0	0	38h
Place cursor	0	0	0	0	0	0	1	1	1	0	0Eh
Clear	0	0	0	0	0	0	0	0	0	1	01h
display											
Write a	1	0		ASCII code for the character (D0=LSB and D7=MSB)							
character											
Move cursor	0	0	1	1	0	0	0	0	0	0	C0h
on line 2											
Move cursor	0	0	1	0	0	0	0	0	0	0	80h
on line 1											
Shift cursor	0	0	0	0	0	1	0	0	0	0	10h
to the left											
Cursor off	0	0	0	0	0	0	1	1	0	0	0Ch
Display off,	0	0	0	0	0	0	1	0	0	0	8h
cursor off											


[11]

After setting the signals for every instruction, the EN signal needs to be put from LOW to HIGH, then after the minimum period again in LOW.

6.3. Implementation in Proteus

 

(fig. 6.3.1: flowchart for functioning of the LCD)

 


(fig. 6.3.2: implementation of LCD in Proteus)

It can be seen that Vdd (power supply) was connected to 5V, typical value from the datasheet, and Vss to ground. Also, the RW pin is connected to ground, as the LCD is used only for writing on it, not for reading from it. RS, RW and the data pins are connected to logic states in order to initialize the LCD and write a text on it. Vee pin is connected to a 20 k Ω potentiometer (typical value taken from datasheet of LM016L) and is used to adjust the brightness.

7. Choosing the microcontroller

The family of microcontrollers chosen for this application is 80C51. These microcontrollers usually have 4x8-bit I/O ports, full-duplex UART (Universal Asynchronous Receiver-Transmitter), 4kx8 internal ROM (program memory), 128x8 internal RAM (data memory), 3x16-bit counters/timers.

 

(fig. 7.1: ports of 8051)

The function of each pin is explained briefly below:


- Vss: ground
- Vcc: power supply
- P0.0...P0.7: I/O ports for address and data bus (low order). If it is used for simple data I/O operations, the pins need to be connected to externally pull-up resistors of $10k\Omega$ when they are used as output pins (because P0 is open drain; without these resistors, the logic level cannot be predicted). If it is used for address/data multiplexing, there is no need for pull-up resistors, as a 74LS373 is connected to latch the addresses.
- P1.0...P1.7: on P1.0 is timer T2 and on P1.1 timer/counter 2 with capture function. The rest are I/O ports.
- P2.0...P2.7: connected to the address bus (higher order addresses).

- P3.0...P3.7: special function registers: RxD (serial input port), TxD (serial output port), INTO (external interrupt), INT1 (external interrupt), T0 (timer 0), T1 (timer 1), WR (external memory write), RD (external memory read)
- RST: it can reset the microcontroller when it is HIGH.
- ALE/PROG (Address Latch Enable/Program Pulse): ALE is used for latching lower order addresses during access to external memory and PROG is used for programming the EPROM.
- PSEN (Program Strobe Enable): external program memory read strobe. Used if memory is accessed for code (external ROM memory). If it is low, a byte pf program code gets on data bus.
- EA/Vpp (External Access Enable/Programming Supply Voltage): if EA is LOW, the microcontroller executes the code from external program memory. If EA is HIGH, the code from internal ROM memory is executed (from addresses 0000h...0FFFh). Vpp receives the program supply voltage during programming the EPROM.
- XTAL1: input to clock generator circuit and inverting oscillating amplifier.
- XTAL2: output from inverting oscillating amplifier. [12]

Several microcontrollers from this family are presented next in comparison, in order to choose one suitable for the application of thermostat system: [1]

No.	Name	RAM	ROM	Voltage	Clock	I/O	ADC	Price (RON)
		size	size	range (V)	frequency	ports	intern	
					(MHz)			
1.	C8051F986-C-GU	512x8	8kx8	1.83.6	25	17	yes	16.53
2.	AT89LP828-20AU	768x8	8kx8	2.45.5	20	30	no	15.15
3.	AT89LP51RB2-	256x8	24kx8	2.45.5	20	40	yes	19.85
	20JU							
4.	AT89LP51-20JU	256x8	4kx8	2.45.5	20	36	no	17.08
5.	AT89LP51RB2-	256x8	24kx8	2.45.5	20	40	yes	18.96
	20AU							


Taking into account all these 5 microcontrollers, there can be seen that all have similar voltage ranges and similar clock frequencies. The difference from the others represents the 1st one, having a smaller voltage range, but no sufficient input/output ports for this application (which requires 26 ports (8 for ADC data, 8 for LCD data, 3 for control ADC, 3 for control LCD, 3 for buttons, 1 for command to heating system)). Taking this aspect into consideration, there can be seen that only the last three ones would be suitable for this application. The 4th one, however, doesn't have an internal ADC and if there is a need to get rid of the external ADC placed in the schematic, this microcontroller wouldn't be suitable. If not, it is the best choice. If the price is taken into consideration and the need for an internal ADC, the **AT89LP51RB2-20AU** would be the best option. The data memory (RAM) and the code memory (ROM) are not factors that influence the decision, as the code and data needed for the application are of small size.

 

(fig. 7.2: the AT89LP51RB2-20AU)


8. Implementing the schematic

8.1. <u>Complete electrical schematic in Proteus</u>

 


(fig 8.1.1: complete schematic)

The data coming from the ADC are connected on P1 (MSB: OUT1 from ADC in P1.7 and LSB OUT8 from ADC in P1.0). Thus, this port needs to be configured from code as being an input port. The command lines for the ADC (Start, EOC, OE) are connected on P3.7, P3.6, P3.5. Port P3.6 is an input port, as from the code the status of the pin EOC needs to be read to know when the conversion finishes. The data lines of the LCD are connected on port P2 (MSB: D7 at LCD in P2.7 and LSB: D0 at LCD in P2.0). The control signals of the LCD (RS, RW, E) are connected on P0.0, P0.1, P0.2. As these pins of the port P0 are used as output pins, pull-up resistors are needed.

 


(fig 8.1.2: crystal oscillator)

There can be seen that at the pins XTAL1 and XTAL 2 a crystal oscillator of frequency 12MHz is connected. The crystal oscillator is very precise and suitable to give the clock frequency for the microcontroller. At XTAL1 there is the input of an inverting oscillating amplifier (internal) and at XTAL2 its output. Consequently, the two capacitors which are connected between the edges of the crystal oscillator and ground have the role to keep the phase of the signal unchanged, because the internal inverting amplifier realizes a phase shift of 180 degrees, the capacitor at the output of XTAL2 together with the crystal oscillator and the other capacitor realize a phase shift of another 180 degrees which means that the clock signal will not suffer any phase shifts. Moreover, the crystal oscillator can also generate beside the fundamental frequency other frequencies which can be filtered out by the capacitors, ensuring a stability in frequency of the oscillator. [13]

 


(fig 8.1.3: buttons)

The buttons to set the desired temperature are connected on P3.2, P3.3, as on these pins external hardware interrupts can be interpreted. There are 2 buttons: PLUS (for increasing the desired temperature), MINUS (for decreasing it). From the schematic, when the buttons are off, at the pins logic '1' is seen. When the buttons get pushed, the corresponding pin gets pushed to GND, so at that pin logic '0' is seen. In this way, the code can be configured in order to know whether a button is pushed or not.

 

(fig 8.1.3: relay)

On pin P0.3, the command to the heating system will be given in form of logic '1' to turn on and '0' to turn off (also pull-up resistor needed because this pin is used as output pin). This command will be given to a transistor that controls the operation of the relay. If the transistor is on (logic '1'), current will flow through the coil that has a magnetic core inside, pushing the metallic arch towards it. In this way, on the anode of the LED will be 5V, so that the LED gets on (and also the heating system that can be connected here, ensuring though a higher voltage for the left circuit part). When the transistor is off, the arch will be pushed away from the coil, turning off the LED.

 

(fig 8.1.4: voltage regulator)

To supply accordingly the devices (LCD, ADC, amplifier, temperature sensor, relay) from the system (with 5V), a voltage regulator that gives at the output 5V is used (it is supplied with a battery of 12V, having decoupling capacitors of 10nF at the input and output).

8.2. Code implementation

First, for displaying a message on the LCD, the settings of the signals that were previously presented need to be made (explanations are in the comments in the code below). To give commands or to display data to the LCD, the busy flag is used. For this, *D7* needs to be read (also *RS* LOW and *RW* HIGH, as there is a read from the LCD and *E* switched from HIGH to LOW). If *D7* is HIGH, it means that the LCD is still busy and if it is LOW, the next operation can be performed. Further, to display the temperature measured by the sensor and converted in digital form by the ADC, the following steps are made:

- First check if the conversion is ready. To do this, on START line a pulse needs to be created, then check if EOC goes from LOW to HIGH (this means end of conversion) and then OE is set HIGH. After that, the data from the output pins can be read and then OE is brought LOW again.
- To find the number: we know we can have from 00h...FFh possible hex values and the range of numbers from 0 to 50.
- To find digit of tens: the numbers 00h...32h correspond to temperatures between 0.00 and 9.08 (ideally is 31h, but experimentally it has been shown that 9.08 is represented by 32h). So, a division by 33h is performed and the quotient represents the digit of tens.
- To find the digit of units: the rest of the previous division has to be taken into consideration. The rest will then be divided by 5h (because there are 5 possible hex values for each unit: e.g.: 0.0, 0.2, 0.4, 0.6, 0.8) and the quotient represents the digit of units.
- To find the digit after the comma: take into consideration the rest of the previous division by 5h and multiply by 2 (as these digits are even numbers) and so the digits after the comma are obtained.

Also, the heater (transistor that drives the relay) is commanded by comparing continuously the real temperature with the desired temperature (digit by digit in ASM and by forming numbers of 3 digits in C). In ASM: the comparison is made by starting from the digit of tens till digit after comma, comparison which is made by dividing the real digits by the desired ones and then the quotient is compared with 0 (meaning that if the quotient is 0, the real digit is smaller than the desired one and if so, the heater is turned on). If the digits are equal, the comparison continues cascaded till digit after comma.

There is also necessary to implement 3 interrupts: one timer interrupt to generate the clock for the ADC (T0) and 2 external hardware interrupts for the two buttons. First, the interrupt enable register needs to be set accordingly to enable the 3 interrupts (0,1,2). The clock for the ADC is designed at a frequency of 100kHz and the timer 0 is used in mode 2 (8-bit timer, auto-charge).

Interrupt 1 is used here. For the buttons, the increment/decrement of temperature is made with a 0.2 step, starting from digit after comma till digit of tens. PLUS button is connected to INTO and MINUS to INT1. For the buttons, the interrupts will be enabled on edge (for this the TCON.0 and TCON.2 bits need to be set).

The display of the real temperature is made continuously on the first row in an infinite loop and the display of the desired temperature is on the second row and is changed only when a button is pressed and after that the cursor is put back to the first row.

A. Code in ASM

```
1
        org 0000h
2
        ljmp main
 3
        org 0003h; INTO interrupt service routine
 4
        ljmp buttonPlus
 5
        org 000Bh; address of interrupt timer 0
 6
        cpl P3.4; pin where the ADC Clock is connected
7
        reti
 8
        org 0013h; INTl interreupt service routine
9
        ljmp buttonMinus
10
11
        org 30h
12
13
   main:
        mov IE, #10000111b; enable INT1, INT0, T0 interrupts
14
15
        acall clockADC
16
        setb TCON.2; enable INT1 when a transition from HIGH in LOW
        setb TCON.O; enable INTO when a transition from HIGH in LOW
17
18
       mov Pl, #0FFh; make Pl input port
19
        ;initial value for desired temperature
20
        mov r3, #2h; digit of tens of desired temp
        mov r4, #1h; digit of units of desired temp
21
22
        mov r5, #4h; digit after comma
23
        mov A, #38h; init LCD
        acall command
24
25
        mov A, #0Eh; place cursor
26
        acall command
        mov A, #01h; clear display
27
        acall command
28
        mov dptr, #1000h; read a string
29
30
        label:
            mov a, #0
31
            movc a, @a+dptr; read letter by letter
32
33
            jz finish
34
            acall display
35
            inc dptr
            sjmp label
36
```

(fig 8.2.1)

```
28
        acall command
29
        mov dptr, #1000h; read a string
30
        label:
31
            mov a, #0
32
            movc a,@a+dptr;read letter by letter
33
            jz finish
34
            acall display
35
            inc dptr
36
            sjmp label
37
        finish:
38
            mov a, #0C0h; force cursor to 2nd line
            acall command
39
40
            mov dptr, #2000h; read the string for desired temperature
41
            labell:
42
                mov a, #0h
43
                movc a,@a+dptr;
44
                jz finishl
45
                acall display
46
                inc dptr
47
                sjmp labell
48
        finishl:
49
            acall shift2ndLineRight
50
            acall displayDesired; display desired temp
51
        convert:
52
            acall shiftlstLineRight; to display real temp
53
            acall findTemp
54
            mov a, #10h; shift cursor to the left to display a new value of the temp
55
            acall command
56
            mov a, #10h
57
            acall command
58
            mov a, #10h
            acall command
59
60
            mov a, #10h
61
            acall command
62
63
            sjmp convert
```

(fig 8.2.2)

```
command:
 65
 66
         acall ready; see if the LCD is ready
 67
         mov P2, A; put command to data lines
         clr P0.0; put RS in 0 for command
 68
         clr P0.1; put R/W in 0 for command
 69
 70
         setb P0.2; put E in 1
 71
         nop
 72
         nop
 73
         clr P0.2; make E H->L
 74
         ret
 75
 76
     display:
 77
         acall ready
 78
         mov P2, A; put data on data lines
 79
         setb PO.O; set RS in 1 for writing
 80
         clr P0.1; put R/W in 0 for writing
 81
         setb P0.2
 82
         nop
 83
         nop
         clr P0.2
 84
 85
         ret
 86
 87
     ready:
 88
         clr P0.2; put E LOW
 89
         nop
 90
         nop
 91
         setb P2.7; make P2.7 (D7) input port
 92
         clr P0.0; put RS in 0 for command register
 93
         setb PO.1; set R/W in 1 for reading
 94
         ; read command register and check busy flag
 95
         back:
 96
              clr P0.2
 97
             nop
 98
             nop
             setb PO.2; switch E L->H and wait for command to be executed
 99
100
              jb P2.7,back;until busy flag is 0
```

(fig 8.2.3)

```
87
    ready:
88
         clr P0.2; put E LOW
89
         nop
90
         nop
91
         setb P2.7; make P2.7 (D7) input port
92
         clr P0.0; put RS in 0 for command register
93
         setb PO.1; set R/W in 1 for reading
94
         ; read command register and check busy flag
95
         back:
96
             clr P0.2
97
             nop
98
             nop
99
             setb P0.2; switch E L->H and wait for command to be executed
             jb P2.7,back;until busy flag is 0
100
101
         clr P0.2
102
         ret
103
104
    readyConversion:
105
         setb P3.7; start the conversion (H->L)
106
         nop
107
         nop
108
         clr P3.7
         setb P3.6; make pin 6 of port 3 input port to read EOC signal
109
110
         ; check if EOC gets low to high
111
         t:
112
             jb P3.6,t
113
         nop
114
         nop
115
         r:
116
             jnb P3.6,r
117
         setb P3.5; set OE High to have the rsult on the output lines
118
         ret
119
120
     findTemp:
121
         acall readyConversion; see if conversion is ready
122
         mov a, P1; take value from ADC
```

(fig 8.2.4)

```
119
120 findTemp:
121
         acall readyConversion; see if conversion is ready
122
         mov a, P1; take value from ADC
        clr P3.5; set OE Low
123
124
125
         mov b, #33h
126
         div ab; divide a by 33h (51 in decimal = 50 possible hex numbers
127 ; that have same tens number + 1 to make the division correct
128 ;e.g. 32h = 50d and is 09.8 degrees, so tens 0) and store in a the quotient
129 ; the quotient is the tens of the temperature number
130
         mov r0,a; save digit of tens
131
         add a, #30h; convert to ASCII
132
         acall display
133
134
         mov a,b;get b
135
         mov b, #5h; divide by 5 beacuse for each unit, there are 5
136 ;possible hex values
137
         div ab
138
         mov rl,a; save digit of units
139
         add a, #30h
140
         acall display
141
142
         mov a, #'.'
143
         acall display
144
145
         mov a,b; get the remainders of the division
146
         mov b, #2h
         mul ab; multiply by 2
147
148 ; beacuse the no after comma are multiples of 2
149 ;store lower 8-bits in a
150
         mov r2, a; save digit after comma
151
         add a, #30h
         acall display
152
153
         acall heater
154
         ret
```

(fig 8.2.5)

```
156
    clockADC:
         ;ADC clock frequency = 100kHz
157
158
         ;T=10us => Ton=Toff=5us
         ;5/1.085 = 5
159
160
         ;load in THO=-5d
         mov TMOD, #02h; mode 2 for timer 0
161
162
         mov THO, #-5d
163
         setb TRO; start timer
164
    ret
165
166
167
    displayDesired:
168
         mov a,r3
169
         add a, #30h
170
         acall display
171
         mov a,r4
172
         add a, #30h
173
         acall display
174
         mov a, #'.'
         acall display
175
         mov a,r5
176
177
         add a, #30h
178
         acall display
179
    ret
180
181
    buttonPlus:
182
    plus:
183
         acall shift2ndLineRight
184
         cjne r3, #5h, below50
185
         acall displayDesired
186
         reti
         below50:
187
         cjne r5, #8h, commaplus
188
189
         cjne r4, #9h, unitsplus
190
         cjne r3, #5h, tensplus
191
         acall displayDesired
```

(fig 8.2.6)

```
180
181
    buttonPlus:
182
    plus:
183
         acall shift2ndLineRight
184
         cjne r3, #5h, below50
185
         acall displayDesired
186
         reti
187
         below50:
188
         cjne r5, #8h, commaplus
         cjne r4, #9h, unitsplus
189
190
         cjne r3, #5h, tensplus
191
         acall displayDesired
192
         reti
193
         commaplus:
194
              inc r5
195
             inc r5
196
              sjmp okl
197
         unitsplus:
198
              inc r4
199
             mov r5, #0h
200
              sjmp okl
201
         tensplus:
202
              inc r3
203
             mov r4, #0h
204
             mov r5, #0h
205
              sjmp okl
         okl:
206
207
208
         acall displayDesired
209
210
    reti
211
212 buttonMinus:
213 minus:
214
         acall shift2ndLineRight
         cjne r5, #0h, commaminus
215
```

(fig 8.2.7)

```
212 buttonMinus:
213 minus:
214
         acall shift2ndLineRight
215
        cjne r5, #0h, commaminus
216
         cjne r4, #0h, unitsminus
         cjne r3, #0h, tensminus
217
218
         acall displayDesired
219
        reti
220
         commaminus:
221
             dec r5
222
             dec r5
223
             sjmp ok
224
         unitsminus:
225
             dec r4
226
             mov r5, #8h
227
             sjmp ok
228
         tensminus:
229
             dec r3
230
             mov r4, #9h
231
             mov r5, #8h
232
             sjmp ok
233
        ok:
234
235
         acall displayDesired
236
237 reti
238
239
     shiftToRightLine:
240
         mov b, #0Ch; jump over the already written message (12 characters)
241
         rightShift:
242
             mov a, #14h
             acall command
243
244
             dec b
245
             mov a,b
         cjne a, #0h, rightShift
246
247
         ret
```

(fig 8.2.7)

```
249
     shiftlstLineRight:
         mov a, #80h; force cursor to 1st line
250
         acall command
251
252
         acall shiftToRightLine
253
254
     ret
255
256
    shift2ndLineRight:
257
         mov a, #0C0h
         acall command
258
259
         acall shiftToRightLine
260
261
    ret
262
263
    heater:
264
         ; divide real temp by desired temp
265
         mov b,r3
         mov a,b
266
267
         jz verifytens; verify divison by 0
268
         mov a,r0
269
         div ab
270
         jnz verifytens; if quotient is 0
271
         ;real temp<desired temp
272
273
         acall turnOnHeater
274
         ret
275
276
         verifytens:
277
         mov a,r0
278
         subb a,r3
279
         jnz goodtemp; if tens are equal, comapare
         ;the units. If not, real temp>desired temp
280
281
282
         units:
283
         ;mov a,rl
284
         mov b, r4
```

(fig 8.2.8)

```
282
         units:
283
         ;mov a,rl
284
         mov b, r4
285
         mov a,b
286
         jz verifyunits; verify divison by 0
287
         mov a,rl
288
         div ab
289
         jnz verifyunits; if quotient 0
290
         ;real temp<desired temp
291
292
         acall turnOnHeater
293
         ret
294
295
         verifyunits:
296
         mov a,rl
297
         subb a,r4
         jnz goodtemp; if units are equal
298
299
         ; verify digit after comma
300
301
         comma:
302
         ;mov a,r2
303
         mov b,r5
304
         mov a,b
305
         jz verifycomma; verify divison by 0
306
         mov a,r2
         div ab
307
308
         jnz verifycomma; if quotient 0
309
         ;real temp<desired temp
310
         acall turnOnHeater
311
312
         ret
313
314
         verifycomma:
315
         mov a,r2
316
         subb a,r5
317
         jnz goodtemp; if digits after
```

(fig 8.2.9)

```
305
        jz verifycomma; verify divison by 0
306
         mov a,r2
307
        div ab
         jnz verifycomma; if quotient 0
308
309
         ;real temp<desired temp
310
311
        acall turnOnHeater
312
        ret
313
314
        verifycomma:
315
        mov a,r2
316
        subb a,r5
317
        jnz goodtemp; if digits after
318
         ;comma are equal => same temp
319
320
        goodtemp:
321
         acall turnOffHeater
322
323 ret
324
325 turnOnHeater:
326
        setb P0.3
327 ret
328
329 turnOffHeater:
        clr P0.3
330
331
    ret
332
333
334 org 1000h
335
         string: db 'Temperature:',0
336
337 org 2000h
        s: db 'Desired: ',0
338
339
340 end
```

(fig 8.2.10)

B. Code in C

```
#include <reg51.h>
1
   sfr lcddata=0xA0; //P2 = LCD D7...D0 pins (A0=address of P2)
2
  sbit RS=P0^0;
3
4 sbit RW=P0^1:
5 sbit EN=P0^2;
6
  sbit busy=P2^7;
7
   sfr adcdata=0x90; //P1 = ADC pins OUT1...OUT8 (90=address of P1)
8
   sbit Start=P3^7:
9
  sbit EOC=P3^6:
10 sbit OE=P3^5;
11 sbit Heater=P0^3;
12 sbit ADCClock=P3^4;
13 sbit EINT1=TCON^2;
14 sbit EINTO=TCON^0:
15
16 code unsigned char string[] = {"Temperature:"};
17 code unsigned char desstring[] = {"Desired:"};
18
  unsigned int a=2,b=1,c=4;//init values for desired temp
19
20 void plusButton();
21 void minusButton();
22
ADCClock = ~ADCClock;
24
25
   }
26
27 - void ButtonMinus() interrupt 2 {//interr for INT1 external
28
     minusButton();
29
   1
30
31 - void ButtonPlus() interrupt 0 {//interr for INTO external
32
     plusButton();
   1
33
34
35 void clockADC();
36 void displayMessage (unsigned char code *dchar);
```

(fig 8.2.11)

```
37 void command(unsigned char value);
38 void ready();
39 void Delay(unsigned int delaytime);
40 void writeToLCD(unsigned char value);
41 void readyConversion();
 42
          void readTemp();
43 void findNumber(unsigned int x);
44 void shiftLineToRight();
45 void shift2ndLineToRight();
46 void shiftlstLineToRight();
47
           void displayDesiredTemp();
48
          void heater(unsigned int x, unsigned int y, unsigned int z);
49 unsigned int formDesiredTemp();
50
51 ⊡void main() {
                 IE=0x87;//enable interr for INTO, INT1, timer 0
52
                 EINT1=1;//enable INT1 when a transition from HIGH in LOW
53
                 EINTO=1;//enable INTO when a transition from HIGH in LOW
54
55
                 clockADC();
56
                 command(0x38);//init LCD
57
                  command(0x0E);//place cursor
58
                 command(0x01);//clear display
59
                 displayMessage(&string);
60
                 command(0xC0);//move in 2nd row
61
                 displayMessage(&desstring);
 62
                  shift2ndLineToRight();
 63
                  displayDesiredTemp();
64 \( \bar{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\tin}\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\tetx{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\text{\te}\text{\text{\text{\text{\text{\text{\text{\text{\text{\texi}\text{\text{\text{\text{\text{\text{\text{\text{\text{\texi}\text{\texit{\text{\texi}\text{\text{\text{\texi}\text{\texit{\text{\tetx{\texi}\text{\texi}\text{\text{\texi}\text{\text{\text{\text{\t
65
                       shiftlstLineToRight();
66
                       readTemp();
 67
                       command(0x10); //shift the cursor to the left 4 positions to display the new value
68
                       command(0x10);
69
                       command(0x10);
70
                        command(0x10);
71
                }
72
           }
```

(fig 8.2.12)

```
73 L
74 - void command(unsigned char value) {
      ready();
76
      1cddata=value;//put on P2 the value of the command
77
78
      RW=0;//prepare to write command
79
      EN=1:
80
     Delay(1);
      EN=0;
81
82
    }
83
84 -void ready() {
85
      EN=0;
86
      busy=1;//make P2.7 input port (D7 of LCD)
87
      RS=0:
88
      RW=1;//prepare to read from LCD
89 🗀
     while(busy==1) {
90
        EN=0;
91
        Delay(1);
92
        EN=1;
93
      }
94
      EN=0;
95
    1
96
97 - void Delay(unsigned int delaytime) {
98
      unsigned int i,j;
99
      for (i=0;i<delaytime;i++)</pre>
      for (j=0;j<1275;j++);//delay of approx 12ms
100
101
    1
102
writeToLCD(*string);
105
106
        string++;
107
     }
108
    }
```

(fig 8.2.13)

```
109
110 - void writeToLCD(unsigned char value) {
      ready();
112
       lcddata=value;
113
      RS=1;
114
      RW=0;//prepare to write
115
      EN=1;
116
      Delay(1);
117
      EN=0;
118
    }
119
120 - void readTemp() {
121
      unsigned int x;
122
      adcdata=0xFF;//input port
123
      readyConversion();//see if cnversion is ready
124
      x=adcdata;
125
      OE=0;//bring OE back to 0
126
      findNumber(x);
127
    1
128
129 - void readyConversion() {
130
      Delav(50);
131
      Start=1;//start the conversion
132
      Delay(1);
133
      Start=0;
134
      EOC=1;//make P3.6 input port
      //check if EOC=LOW to HIGH -> ready conversion
135
137
        }
138
      while (EOC!=1) {
139 -
        }
140
      OE=1;//set OE to 1 to put result on output lines
141
      Delay(1);
142
    }
143
144 - void findNumber (unsigned int x) {
```

(fig 8.2.14)

```
142 }
143
144 — void findNumber (unsigned int x) {
145
       unsigned int y;
146
       unsigned int d,e,f;//to save real temp
       d=x/51;//save digit of tens
147
148
      v=x%51;
149
      e=v/5;//save digit of units
150
      writeToLCD(d+0x30);//digit of tens
151
      writeToLCD(e+0x30);//digit of units
152
      writeToLCD(0x2E);//put the dot
      y=x%0x33;
153
154
      v=v%0x05;
      y=y*0x02;//digit after comma, only even
155
      f=y;//save digit after comma
156
      writeToLCD(v+0x30);
157
158
      heater(d,e,f);
159
    1
160
161 \( \subseteq \text{void clockADC() } \) {
       //ADC clock frequency = 100kHz
162
163
      //T=10us => Ton=Toff=5us
      //5/1.085 = 5
164
      //load in THO=-5d
165
      TMOD=0x02;//mode 2 for timer 0
166
167
      TH0=-5:
      TRO=1;//start timer 0
168
169
170
171 \( \subseteq \text{void shiftLineToRight(){}} \)
172
      unsigned int i;
173
      for (i=0;i<12;i++) {
174
         command(0x14);//jump over 12 positions
175 - }
176
    }
177
```

(fig 8.2.15)

```
178 - void shift2ndLineToRight() {
179
       command(0xC0);//start of 2nd line
180
       shiftLineToRight();
181
     1
182
183 - void shiftlstLineToRight() {
184
       command(0x80);
185
       shiftLineToRight();
186
     }
187
188
189 \( void \) displayDesiredTemp() {//write the desired temp
190
       writeToLCD(a+0x30);
191
       writeToLCD(b+0x30);
192
       writeToLCD('.');
193
      writeToLCD(c+0x30);
194
    }
195
196 

— void heater (unsigned int d, unsigned int e, unsigned int f) {
197
       unsigned int x;
198
       x=formDesiredTemp();//form number corresp to desired temp
199
       d*=100:
200
       e*=10;
201
       d=d+e;
202
       d=d+f;//form number corresp to real temp
203
       if (d<x)
204
         Heater=1;
205
       else
206
         Heater=0;
207
    1
208
209 \( \sum \text{unsigned int formDesiredTemp() {
210
       unsigned int x, y, z;
211
       x=a;
212
       v=b;
213
       z=c;
```

(fig 8.2.16)

```
209 \( \sum \text{unsigned int formDesiredTemp() {
210
       unsigned int x,y,z;
211
       x=a;
212
      y=b;
213
      z=c;
214
      x*=100:
215
      y*=10;
216
      x=x+y;
217
      x=x+z;
218
      return x;
219 }
220
221 - void plusButton() {
       shift2ndLineToRight();
       if(a<5){//verify if max is not reached
223
224
         if (c!=8)//if comma hasn't reached max value, increment
225
           c+=2;
226
         else//else increment unit
           if (b!=9) {//if units hasn't reached max value
227
228
             c=0;//put comma in 0
229
             b++;
230
           1
231
           else
232
             if (a!=5) {//if tens hasn't reached max value
233
               b=0;//reset units
234
               c=0;//reset comma
235
               a++;
236 -
             }
237
238
      displayDesiredTemp();
239
240 -
241 - void minusButton() {
242
       shift2ndLineToRight();
243
       if (c!=0)//if comma is not zero, decrement
244
         c-=2;
```


(fig 8.2.17)

```
223 🗀
       if(a<5){//verify if max is not reached
224
         if (c!=8)//if comma hasn't reached max value, increment
225
           c+=2;
226
         else//else increment unit
           if (b!=9) {//if units hasn't reached max value
227
228
             c=0;//put comma in 0
229
             b++;
230 -
231
           else
232
             if (a!=5) {//if tens hasn't reached max value
233
              b=0://reset units
234
               c=0;//reset comma
235
               a++;
236
             }
237
      1
238
      displayDesiredTemp();
239
    }
240
241 - void minusButton() {
242
       shift2ndLineToRight();
243
      if (c!=0)//if comma is not zero, decrement
244
         c-=2;
245
       else//else decr units
246
        if (b!=0) {//if units hasn't reached min value
247
           c=8;//reset comma
248
          b--;//decr units
249 -
         1
250
         else
251 🗀
          if (a!=0) {//if tens hasn't reached min value
252
             c=8://reset comma
             b=9;//reset units
253
254
             a--;//decr tens
255
256
      displayDesiredTemp();
257
    }
258 -
```

(fig 8.2.18)

8.3. <u>Simulation</u>

- At the temperature of 21.2°C

 

(fig 8.3.1: simulation)

9. References

- 1. https://ro.mouser.com/?gclid=EAlaIQobChMI_6HP5Orn_QIVh5XVCh2cFQnsEAAYASAAE gljGPD BwE
- 2. https://atlas-scientific.com/blog/how-do-temperature-sensors-work/
- 3. https://www.rotronic.com/en-us/humidity_measurement-feuchtemessungmesure de l humidite/capacitive-sensors-technical-notes-mr
- 4. https://www.electronicshub.org/humidity-sensor-types-working-principle/#Thermal Conductivity Humidity Sensors
- 5. https://www.allaboutcircuits.com/textbook/digital/#chpt-13
- 6. http://www.edutecnica.it/elettronica/datasheets/DAC-ADC/ADC0808.pdf
- 7. https://www.ti.com/cn/lit/ds/symlink/lm45.pdf?ts=1681022156418&ref_url=https%253 A%252F%252Fwww.google.com%252F
- 8. https://www.alldatasheet.com/view.jsp?Searchword=Ad8603&gclid=Cj0KCQjwxMmhBh DJARIsANFGOSt6W-
- 9. https://www.javatpoint.com/what-is-lcd
- 10. LCD 16×2 (LM016L) « Innovation of Engineers (wordpress.com)
- 11. HD44780 pdf, HD44780 Download, HD44780 Description, HD44780 Datasheet, HD44780 view ::: ALLDATASHEET :::
- 12. Microcontrollers courses
- 13. https://www.edaboard.com/threads/why-do-we-connect-capacitors-to-the-crystal-in-the-microcontroller.259887/